

EE230: Labwork-8

Logarithmic Amplifier

Kalpiti Borkar, 200070029

March 20, 2022

1 Overview of the experiment

1.1 Aim of the experiment

To understand the structure and workings of logarithmic amplifier by:

1. Observing the $\ln(I_D)$ vs V_D plot.
2. Constructing the model in NGSpice
3. Theoretical analysis

1.2 Methods

Firstly, we plotted the $\ln(I_D)$ vs V_D data, which was provided to us. Next, we identified the linear region and thus parameters like I_s and n . Next we determined the values of V_{offset} , R_1 , R_2 and R_3 followed by simulating the model in NGSpice and fine-tuning.

2 Design

The 4-stage logarithmic amplifier consists of 4 blocks as shown in figure 1 below:

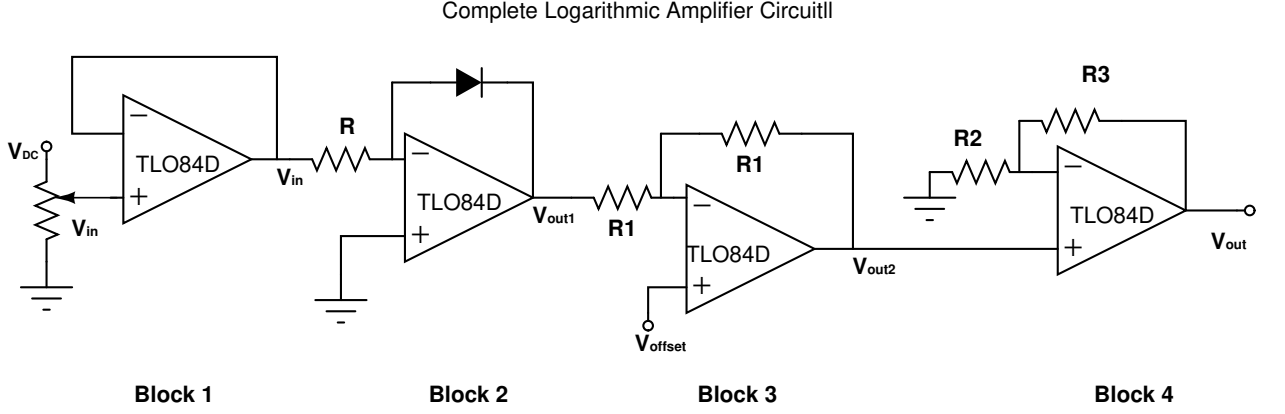


Figure 1: 4-stage logarithmic amplifier

Voltage is converted into current, which is forced through a diode in block 2.

$$I_D = \frac{V_{in}}{R} \quad (1)$$

By theoretical analysis:

$$V_{out1} = a_1 \ln(V_{in}) + a_2 \quad (2)$$

$$a_1 = -nV_T \quad (3)$$

$$a_2 = nV_T \ln(I_S R) \quad (4)$$

Block 3 is used to remove the offset voltage with value a_2 from output voltage V_{out1} .

$$V_{out2} = -a_1 \ln(V_{in}) - a_2 + 2V_{offset} \quad (5)$$

Block 4 is used to scale the output voltage V_{out2} by a factor of a_2 , thus giving us the true natural logarithm of V_{in} .

$$V_{out} = -a_1(1 + \frac{R_3}{R_2})\ln(V_{in}) \quad (6)$$

Then choose:

$$\frac{1}{1 + R_3/R_2} = -a_1 \quad (7)$$

$$\therefore V_{out} = \ln(V_{in}) \quad (8)$$

3 Experimental results

3.1 Part-1

$\ln(I_D)$ vs V_D plot:

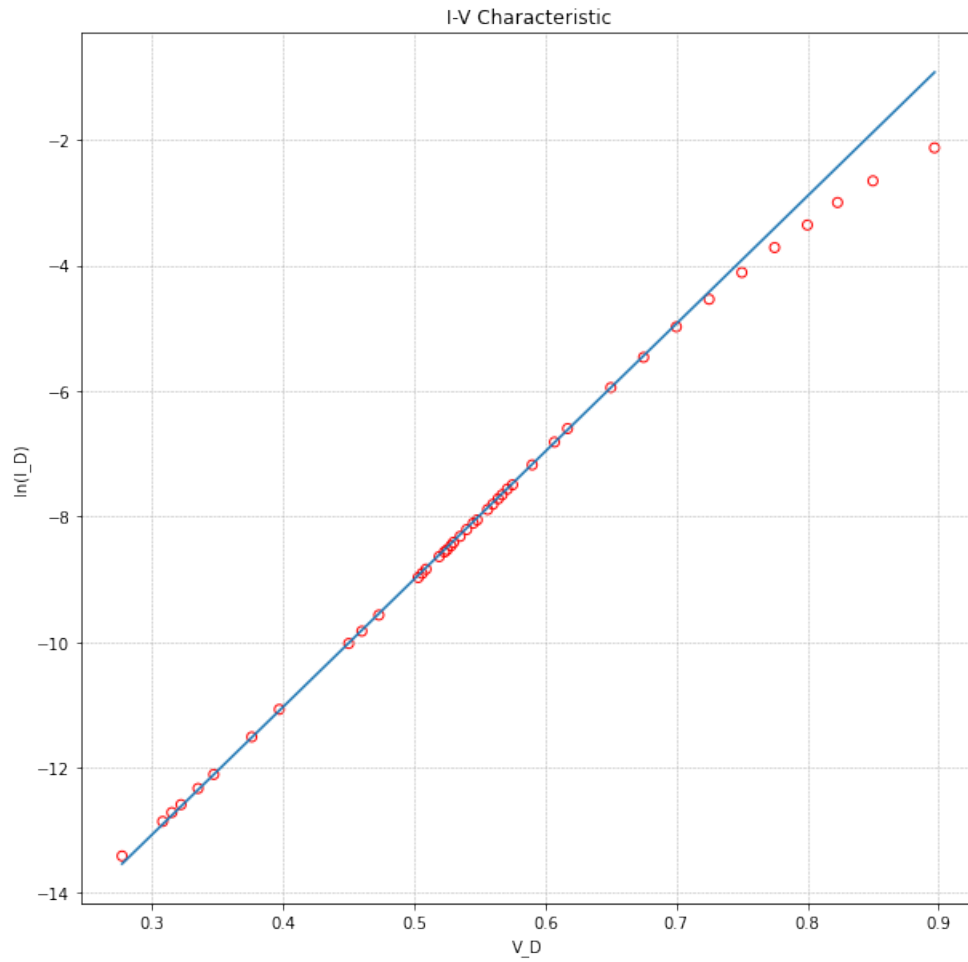


Figure 2: $\ln(I_D)$ vs V_D

3.2 Part-2

Observe that the graph is linear in the region between $V_D = 0.315$ and $V_D = 0.7$

Equation of the line passing through these two points is:

$$\ln(I_D) = 20.1V_D - 19 \quad (9)$$

$$\therefore n = 1.91 \quad (10)$$

$$\therefore I_S = 5.6 * 10^{-9} \quad (11)$$

3.3 Part-3

From figure 2 given above, $\ln(I_{D2}) = -4.11$.

$$\therefore R = \frac{10}{I_{D2}} = 612 \text{ohms} \quad (12)$$

3.4 Part-4

$$V_{out1} = -0.0497\ln(V_{in}) - 0.626 \quad (13)$$

3.5 Part-5

$$V_{offset} = -0.313V \quad (14)$$

$$R_1 = 1\text{k ohm}$$

$$\frac{1}{1 + R_3/R_2} = -a_1 \quad (15)$$

$$\therefore \frac{R_3}{R_2} = 19.1 \quad (16)$$

Choose: $R_1 = 19.1\text{k ohm}$

$R_1 = 1\text{k ohm}$

3.6 Part-67

Netlist code:

```
lab8

.include 1N4148.txt
.include TL084.txt

vin 1 0 1

r0 1 2 612
r11 5 6 1k
r12 6 10 1k
r21 11 0 1000
r31 11 14 18k

v3 3 0 12
v4 4 0 -12

v8 8 0 12
v9 9 0 -12

v12 12 0 12
v13 13 0 -12

* v7 7 0 -0.391
v7 7 0 -0.3047

x1 0 2 3 4 5 TL084
x2 7 6 8 9 10 TL084
x3 10 11 12 13 14 TL084

D1 2 5 1N4148

.dc vin 0.1 10 0.1
```

```

.control
run
plot v(14) vs ln(v(1))
* print v(14) vs v(1)

```

3.7 Part-8

V_{out} vs V_{in} :

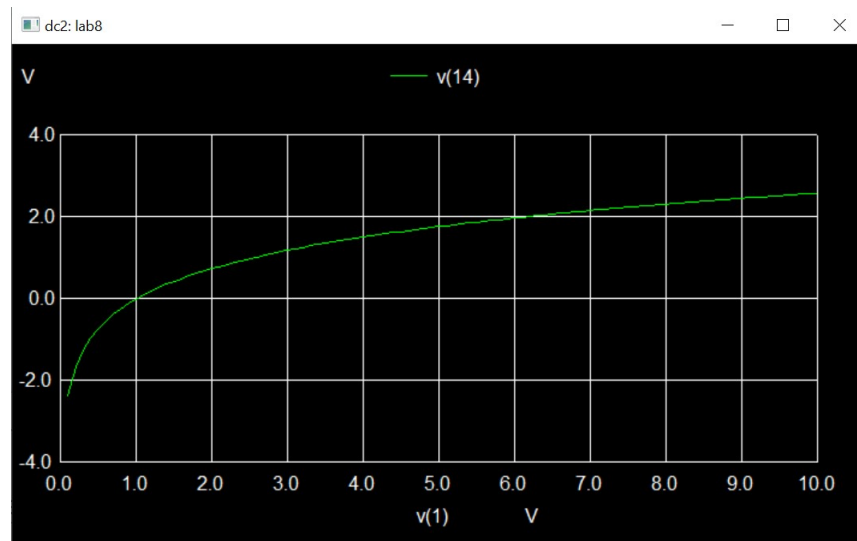


Figure 3: V_{out} vs V_{in}

V_{out} vs $\ln(V_{in})$:

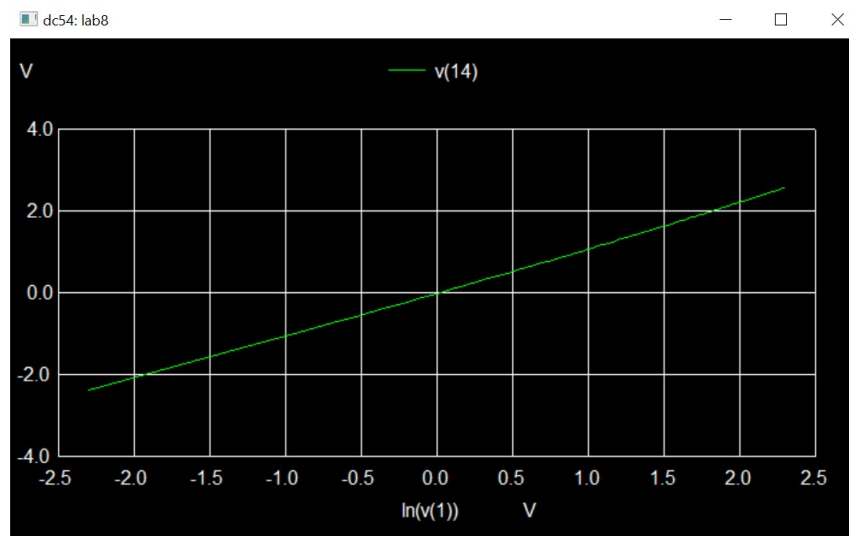


Figure 4: V_{out} vs $\ln(V_{in})$