

EE230: Labwork-9

Instrumentation Amplifier on load cell sensor

Kalpiti Borkar, 200070029

April 4, 2022

1 Overview of the experiment

1.1 Aim of the experiment

To implement instrumentation amplifier to amplify output from a load cell sensor by:

1. Building instrumentation amplifier using TL084 IC.
2. Implementing instrumentation amplifier using INA128 IC.

1.2 Methods

In this experiment, we design a circuit to measure the weight of any object. We achieve the same by using a load cell and an instrumentation amplifier. The load cell is based on Wheatstone bridge and the arrangement allows us to measure very small in resistance R .

2 Design

In this experiment, we are going to construct a circuit consisting of the load cell as well as the instrumentation amplifier.

The load cell is based on the Wheatstone bridge and changes its resistance on exposure to physical deformation.

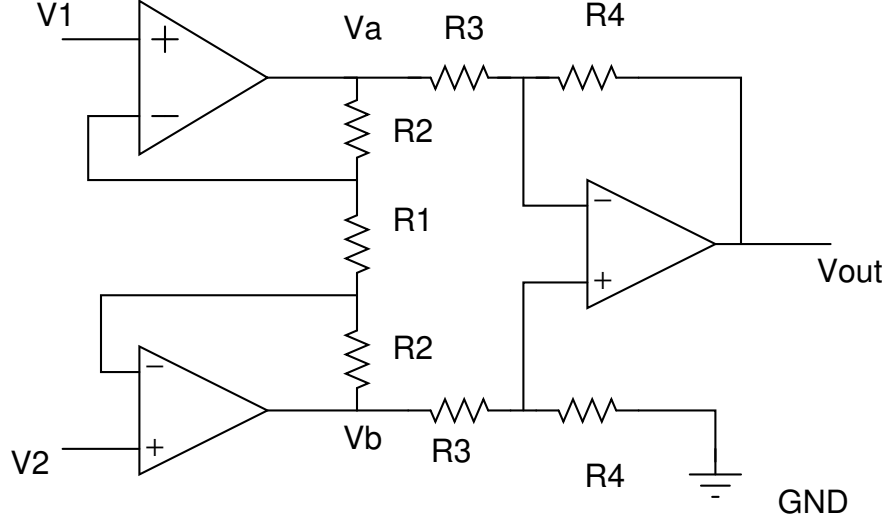


Figure 1: Instrumentation amplifier

The instrumentation amplifier consists of three amplifiers as shown in the figure 1 above. It is a type of differential amplifier used to achieve high accuracy and stability.

3 Theory

Applying KCL on the input of op-amps:

$$V_a = V_1(1 + \frac{R_2}{R_1}) + V_2(\frac{R_2}{R_1}) \quad (1)$$

$$V_b = -V_1(\frac{R_2}{R_1}) + V_2(1 + \frac{R_2}{R_1}) \quad (2)$$

From the above two equations and using superposition theorem:

$$V_{out} = \frac{R_4}{R_3}(1 + 2\frac{R_2}{R_1})(V_2 - V_1) \quad (3)$$

Therefore, we get the gain as follows:

$$A_v = \frac{R_4}{R_3}(1 + 2\frac{R_2}{R_1}) \quad (4)$$

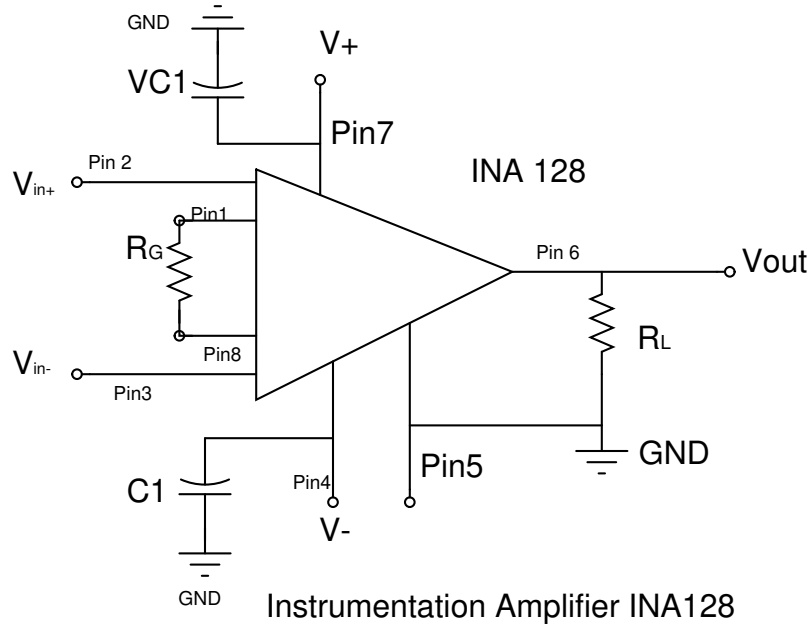


Figure 2: INA128

Selecting the values of resistors for part-1:

The load resistance was taken as **10k ohms**

In order to obtain a gain of 300,

$$A_v = \frac{R_4}{R_3} \left(1 + 2 \frac{R_2}{R_1} \right) = 300 \quad (5)$$

Choosing:

$$R_1 = 1k\text{ohms} \quad (6)$$

$$R_2 = 1k\text{ohms} \quad (7)$$

$$R_3 = 1k\text{ohms} \quad (8)$$

$$R_4 = 100k\text{ohms} \quad (9)$$

Selecting the values of resistors for part-3:

$$R_G = 220\text{ohms} \quad (10)$$

$$R_L = 10k\text{ohms} \quad (11)$$

4 Experimental results

$$sensitivity = \frac{V_2 - V_1}{W_2 - W_1} V/gm \quad (12)$$

4.1 Part-1

$V_{out}(V)$ vs Weights(grams)

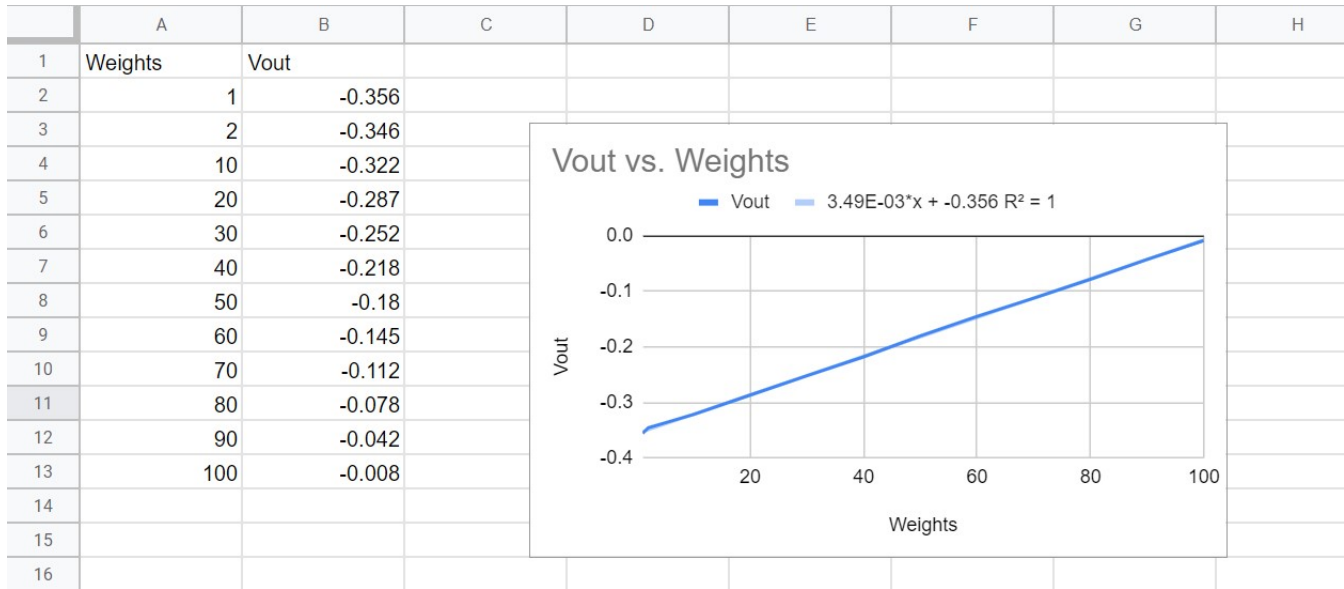


Figure 3: $V_{out}(V)$ vs Weights(grams)

The observed sensitivity in mV/gm from the above graph is:**3.29** We need to find the value of R_1 such that the sensitivity doubles.

On adjusting the value of R_1 to double the sensitivity, we obtained a value of:

$$R_1 = 400ohms \quad (13)$$

Where R_1 was initially 1k ohms.

4.2 Part-3

$V_{out}(V)$ vs Weights(grams)

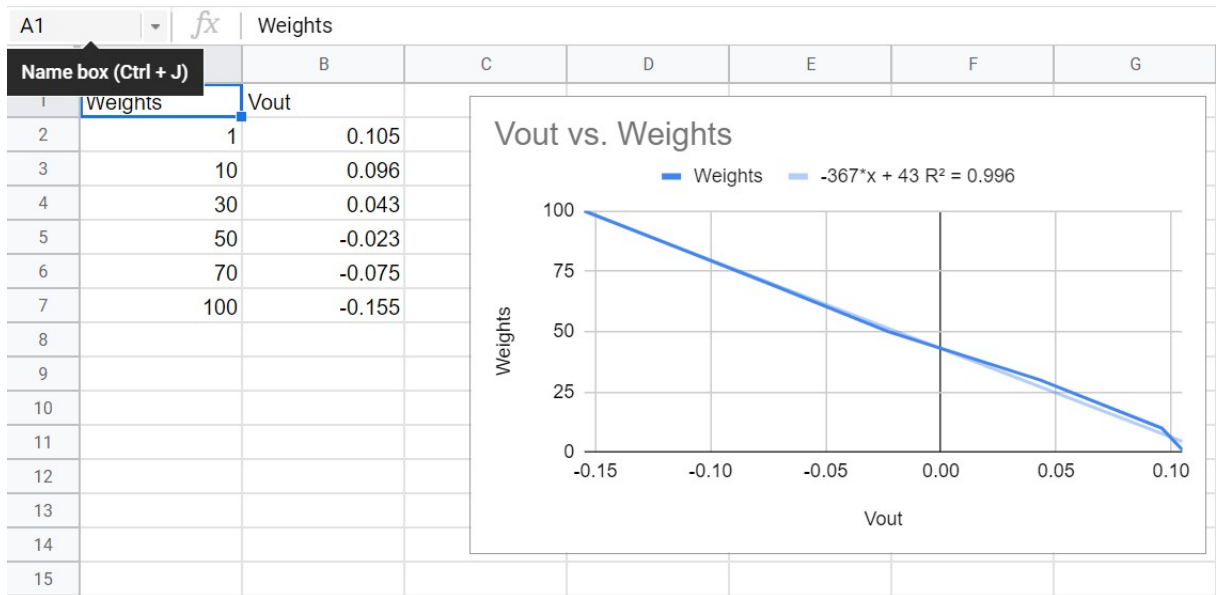


Figure 4: $V_{out}(V)$ vs Weights(grams)

The observed sensitivity in mV/gm from the above graph is:-**0.367**

$V_{out}(V)$ vs Weights(grams):

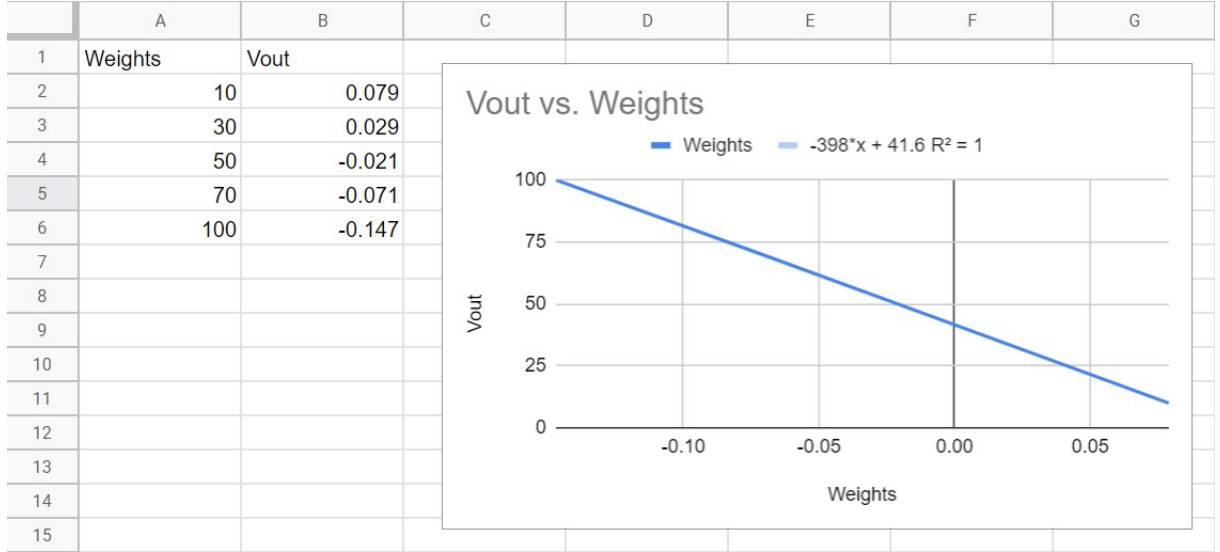


Figure 5: $V_{out}(V)$ vs Weights(grams)

Here, we were asked to adjust the value of R_g to obtain a sensitivity of -0.4. The observed sensitivity in mV/gm from the above graph is: **-0.398** We need to adjust the value of R_G such that the sensitivity doubles: By adjusting the potentiometer, we found the value of R_G to be 102 ohms, which was initially 220 ohms.

Conclusion:

The output voltage V_{out} varies linearly with the weights placed on the load cell as can be observed from the plots above.

5 Experiment completion status

All parts of the experiment were successfully completed (part-1 and part-3) and various parameters were recorded for making observations.